

Dadda multiplier algorithm:

1. First partial products are generated using multiplier and multiplicand as they are available at same time at $t=0$.


2. collecting the partial products bits with the same place value in groups of wires and reducing these in several layers till only 2 wires are left in each weight.

3. at last these 2 wires in each weight are added with a fast adder like Brent-Kung etc.

Layer reduction technique:

In dadda algorithm, we come from last layer in which we only need to have 2 bits. and the last before stage are allowed to have $\leq \left\lceil \frac{3}{2} (\text{last stage bits}) \right\rceil$. like wise we come all the way to first layer.

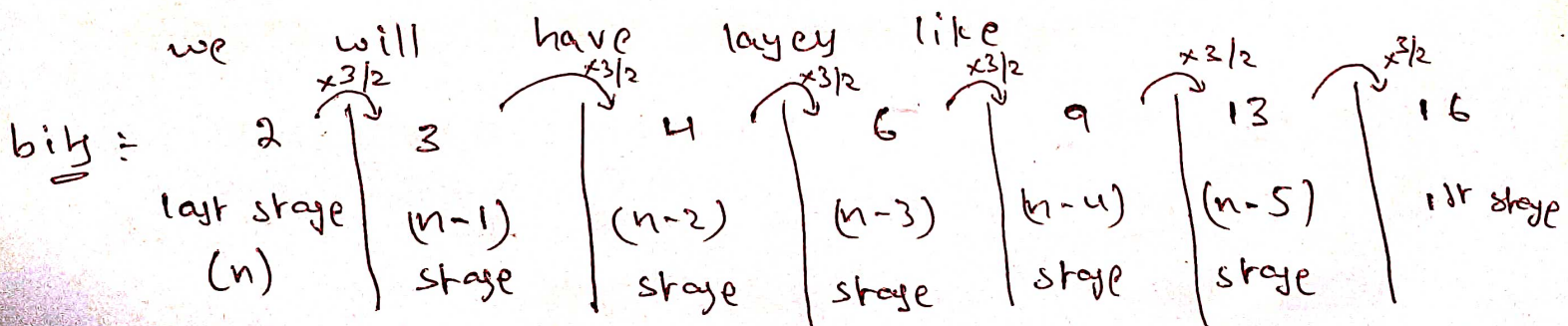for example if we have 16 bit multiplier,




So total, we have 7 stages.

In last stage, we have 32 bits of 2 rows each, we just give these bits to a Brent kung adder for fast addition. If we want to reduce 3 bits to 2 bits, we use a full adder and ~~per~~ it produces a sum in the same weight and carry in the higher weight.

The below example can give a better understanding with the help of dot diagram.

4x4 multiplication:

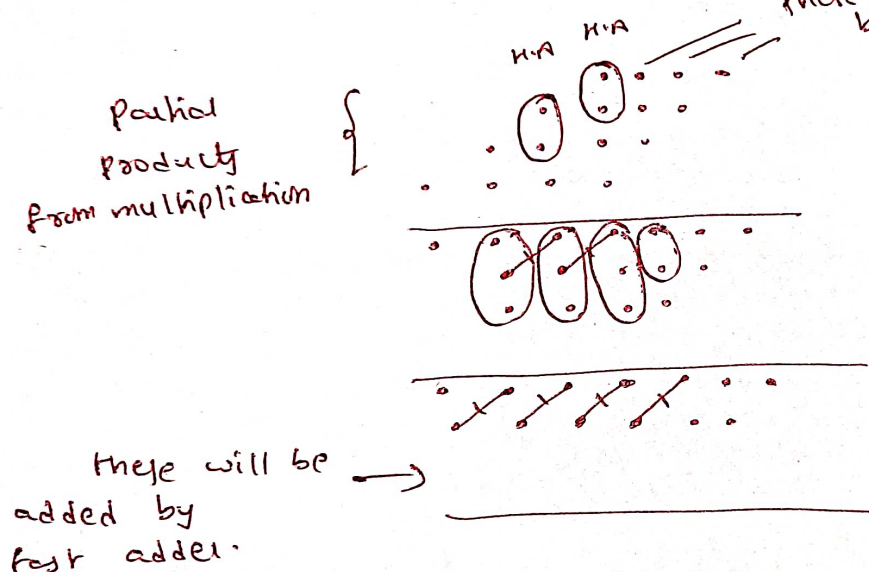

there will be passed to next layer as it is because they are ≤ 3 .

capacity = 4 \Rightarrow next stage capacity = $4 \times \frac{2}{3} = 3$

capacity = 3 \Rightarrow next stage capacity = $3 \times \frac{2}{3} = 2$

capacity = 2

In the first layer, we know second layer capacity is 3 bits at each weight. So we use a half adder to reduce by 1 bit but we have to take care that an extra bit will be added to current weight if a full adder or adder is used at the previous weight.

16x16 dot adder multiplier reduction by dot diagram;

⊖ → half adder
⊕ → full adder

30 29 28 27 26 25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1 0

Stage 1:
capacity = 16.

Partial
Products
obtained
by multipli
and multipli
and.

Stage-2
capacity
= 13

Stage 3
capacity = 9


Stage 4
capacity = 6

Stage 5
capacity = 4

Stage 6
capacity = 3

Stage 7
capacity = 2

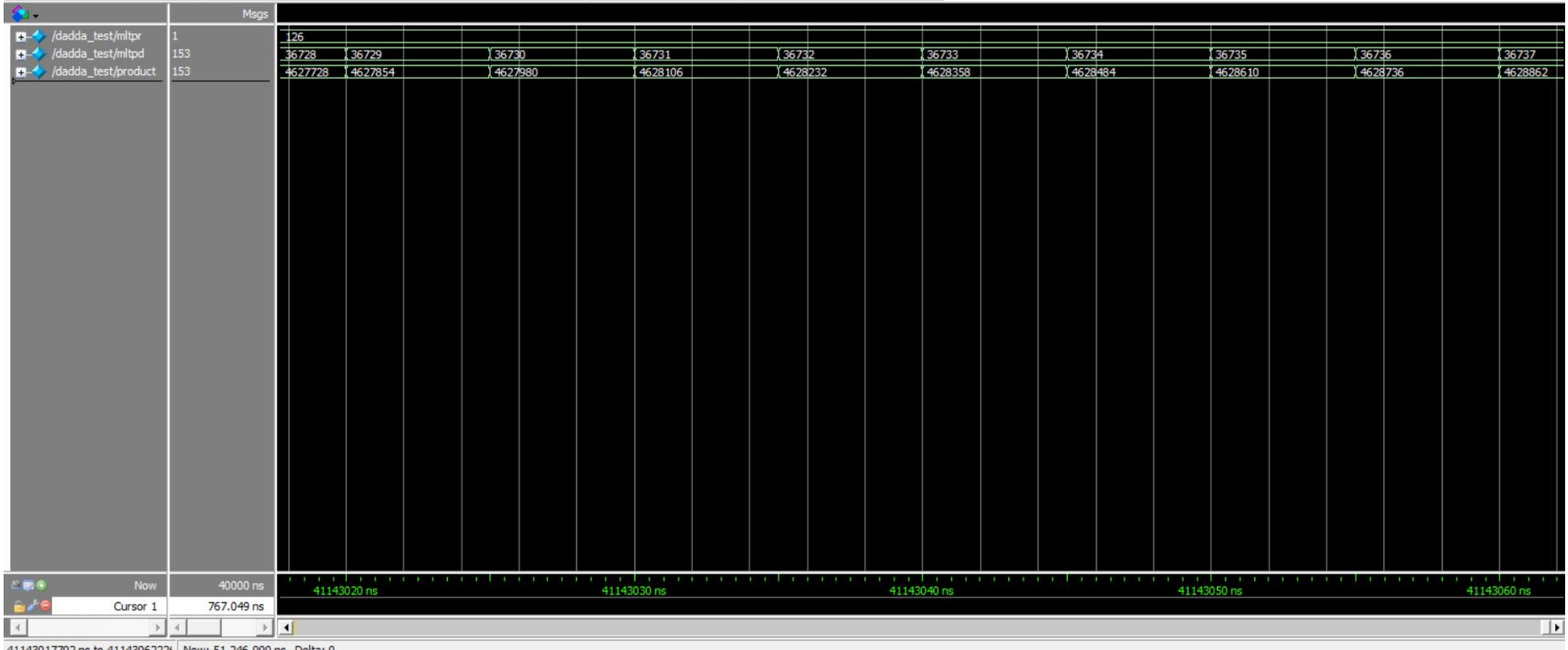last stage to Brent-Kung adder to produce product //



[illegible]